
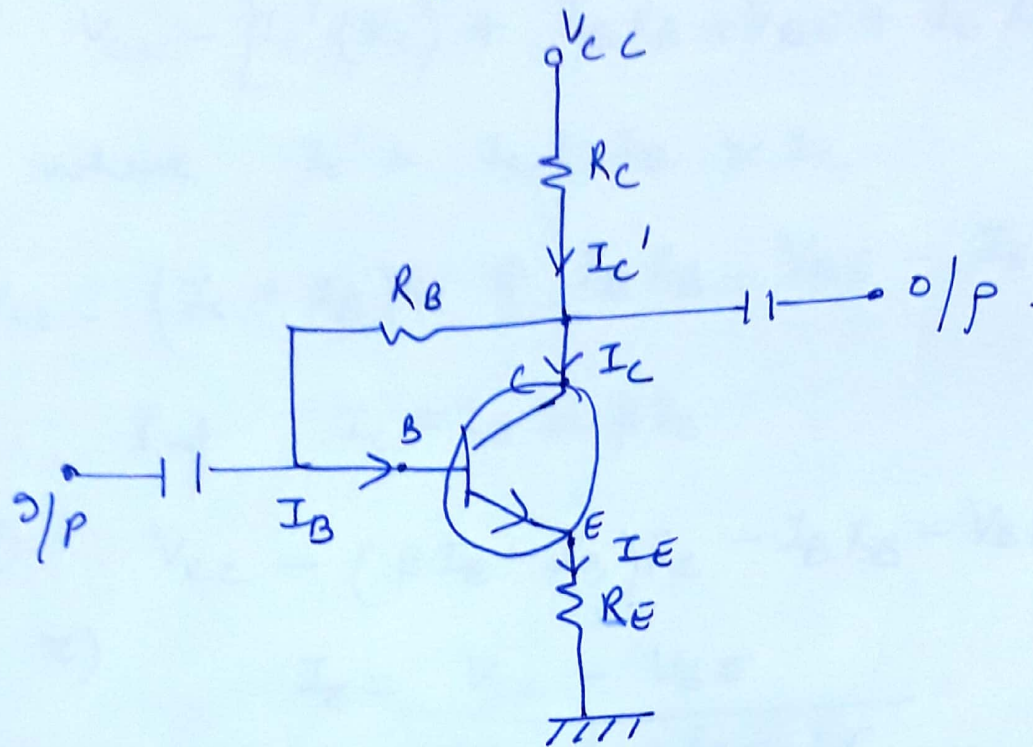


Collector feedback Configuration

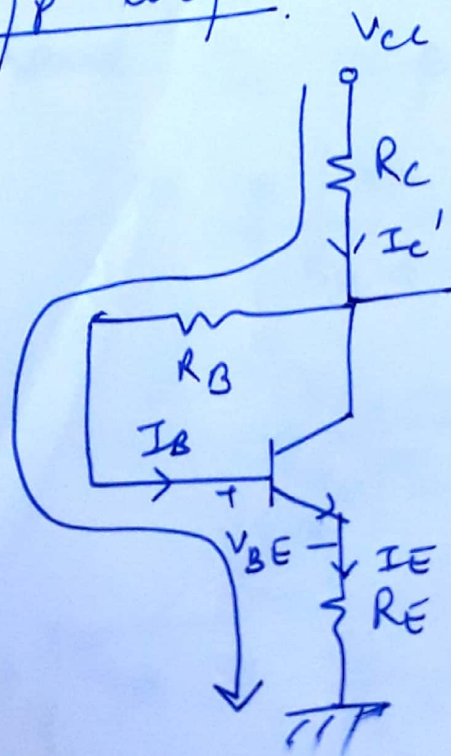

To find operating points

① o/p loop



Applying KVL.

$$V_{CC} - [I_C'(R_C) + I_B R_B + V_{BE} + I_E R_E] = 0.$$

where $I_C' = I_C + I_B \approx I_C$.

$$V_{CC} - (I_C + I_B)R_C - I_B R_B - V_{BE} - I_E R_E = 0.$$

Put $I_C \approx I_E = \beta I_B$.

$$\Rightarrow V_{CC} - (\beta I_B + I_B)R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1)R_C + R_B + \beta R_E}$$

take $\beta + 1 \approx \beta$.

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

we have $I_C = \beta I_B$.


$$= \frac{\beta (V_{CC} - V_{BE})}{R_B + \beta(R_C + R_E)}$$

$$= \frac{V_{CC} - V_{BE}}{\cancel{\frac{R_B}{\beta}} + (R_C + R_E)}$$

$$\Rightarrow \boxed{I_{CQ} \approx \frac{V_{CC} - V_{BE}}{R_C + R_E}} \quad \left(\text{Independent of } \beta \right)$$

(2)

Output loop

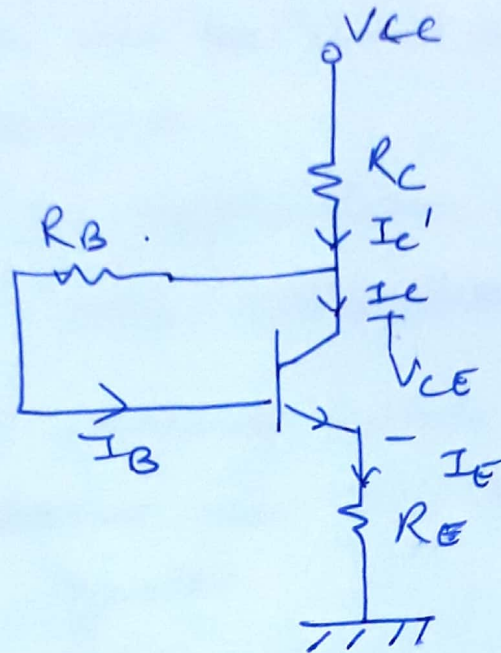

Applying KVL.

$$V_{CC} - I_{C'} R_C - V_{CE} - I_E R_E = 0$$

$$\text{or } V_{CC} - I_E R_C - V_{CE} - I_E R_E = 0$$



$$\text{or } \boxed{V_{CE} = V_{CC} - I_E (R_C + R_E)}$$

Transistor as a switch


Transistor can be used as an amplifier as well as a switch.

For switching application, it is biased to operate in the saturation or cutoff regions.

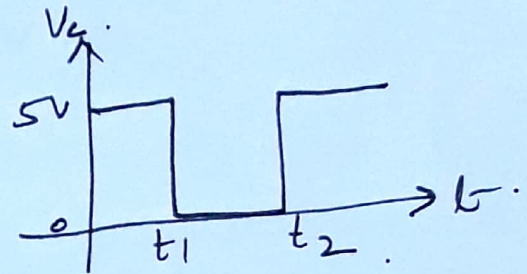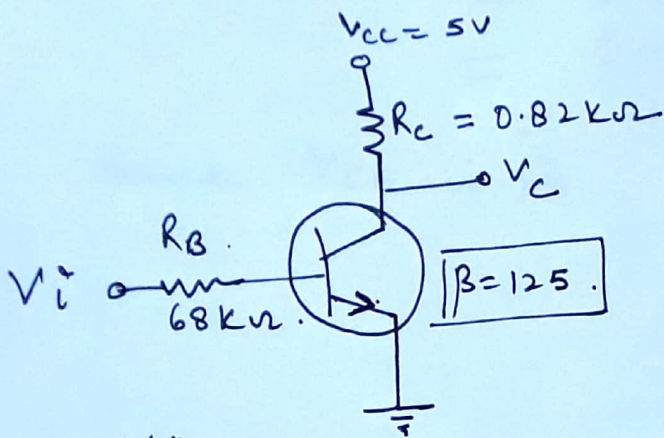Note:- for making switch, the d.c. supply is absent from the base circuit.



where V_i is

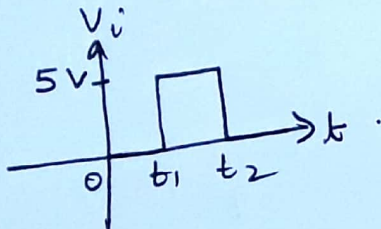


Working 1: (Transistor as an 'open' switch)

For $(0 \text{ to } t_1)$ $V_i \rightarrow 0 \Rightarrow I_B = 0$ and hence $I_C = 0$.

(BE junction is reverse bias)

(The transistor works in Cutoff region as both junctions are reverse bias)

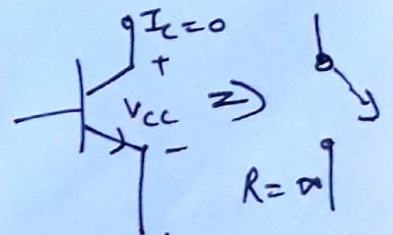Q points \rightarrow
$$\begin{matrix} I_C = 0 \\ V_{CE} = V_{CC} \end{matrix}$$




2) Transistor act as a closed switch.

When $V_{in} = 5V$ (from t_1 to t_2).

The transistor works in saturation region as both the junctions will be forward biased.

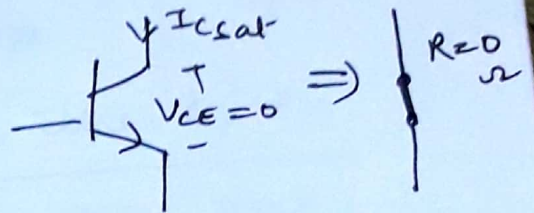In saturation condition we take $V_{CE} \approx 0V$.



$$\Rightarrow I_C = \frac{V_{CC}}{R_C}$$

\downarrow
 I_{Csat}


so. $I_{Csat} = \frac{V_{CC}}{R_C}$

For successful implementation of the transistor in saturation, make sure that

$$I_B > \frac{I_{Csat}}{\beta}$$

$$\text{or } I_{Bmax} \approx \frac{I_{Csat}}{\beta}$$


(in active)

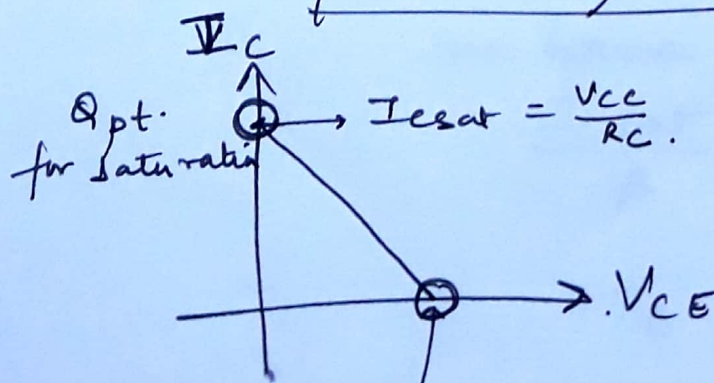

Q. pt for cutoff.

$$V_{CEcutoff} = V_{CC}$$

Numerical for Transistor as a switch.

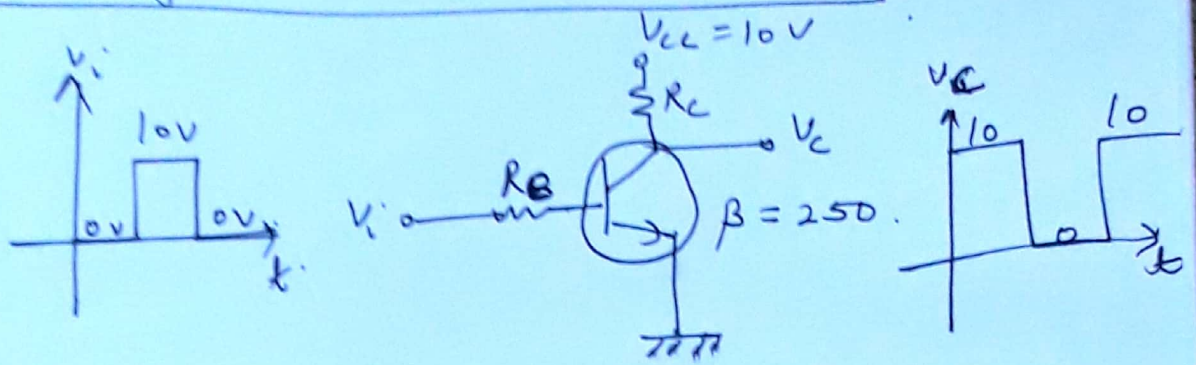

determine R_B and R_C for the N/w.

$$\text{if } I_{Csat} = 10 \text{ mA}$$

Solⁿ we have

$$I_{Csat} = \frac{V_{CC}}{R_C}$$

$$\Rightarrow 10 = \frac{10}{R_C}$$

$$\Rightarrow R_C = 1 \text{ k}\Omega$$

for saturation

$$I_B > \frac{I_{Csat}}{\beta}$$

we have

$$\frac{I_{Csat}}{\beta} = \frac{10}{250} = 0.04 \text{ mA}$$

$$\Rightarrow I_B > 0.04 \text{ mA}$$

$$\therefore \frac{V_{in} - 0.7}{R_B} > 0.04 \text{ mA}$$

$$\Rightarrow R_B < \frac{10 - 0.7}{0.04} = 232.5 \text{ k}\Omega$$