

# **Operational Amplifier**

**P. Bachan  
Assistant Professor  
Dept. of ECE  
GLA University**

# Operational Amplifier




## Applications:

Addition  
Subtraction  
Integration  
Differentiation

Active Filters  
Oscillator  
Waveform Converter  
ADC and DAC


# Basic Op-Amp

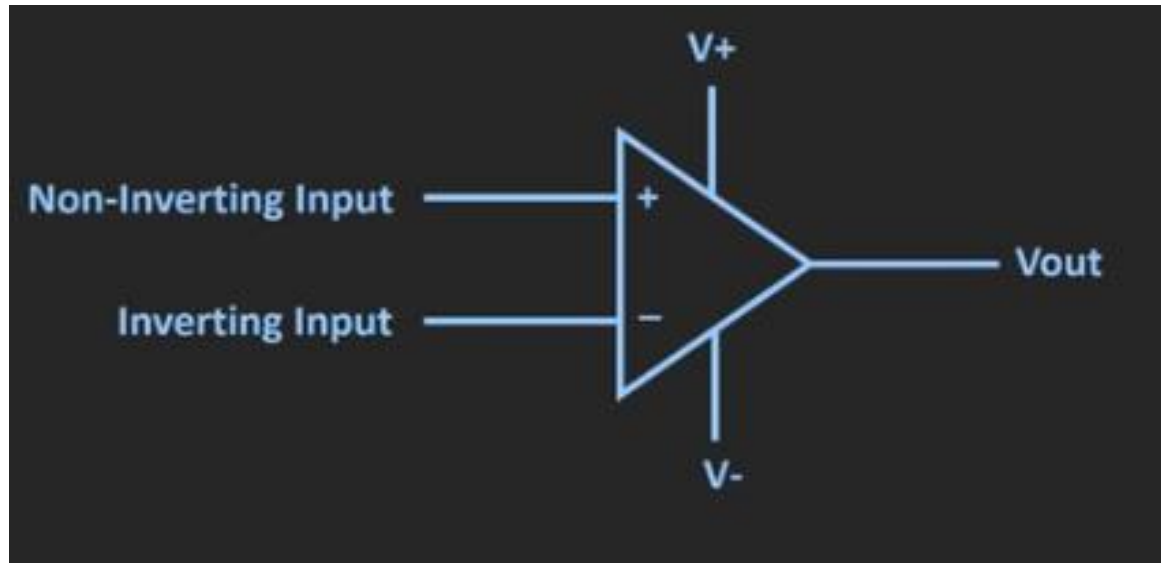


Operational amplifier or op-amp, is a very high gain differential amplifier with a high input impedance (typically a few meg-Ohms) and low output impedance (less than 100  $\Omega$ ).

Note the op-amp has two inputs and one output.


# Non-Inverting Op-AMP

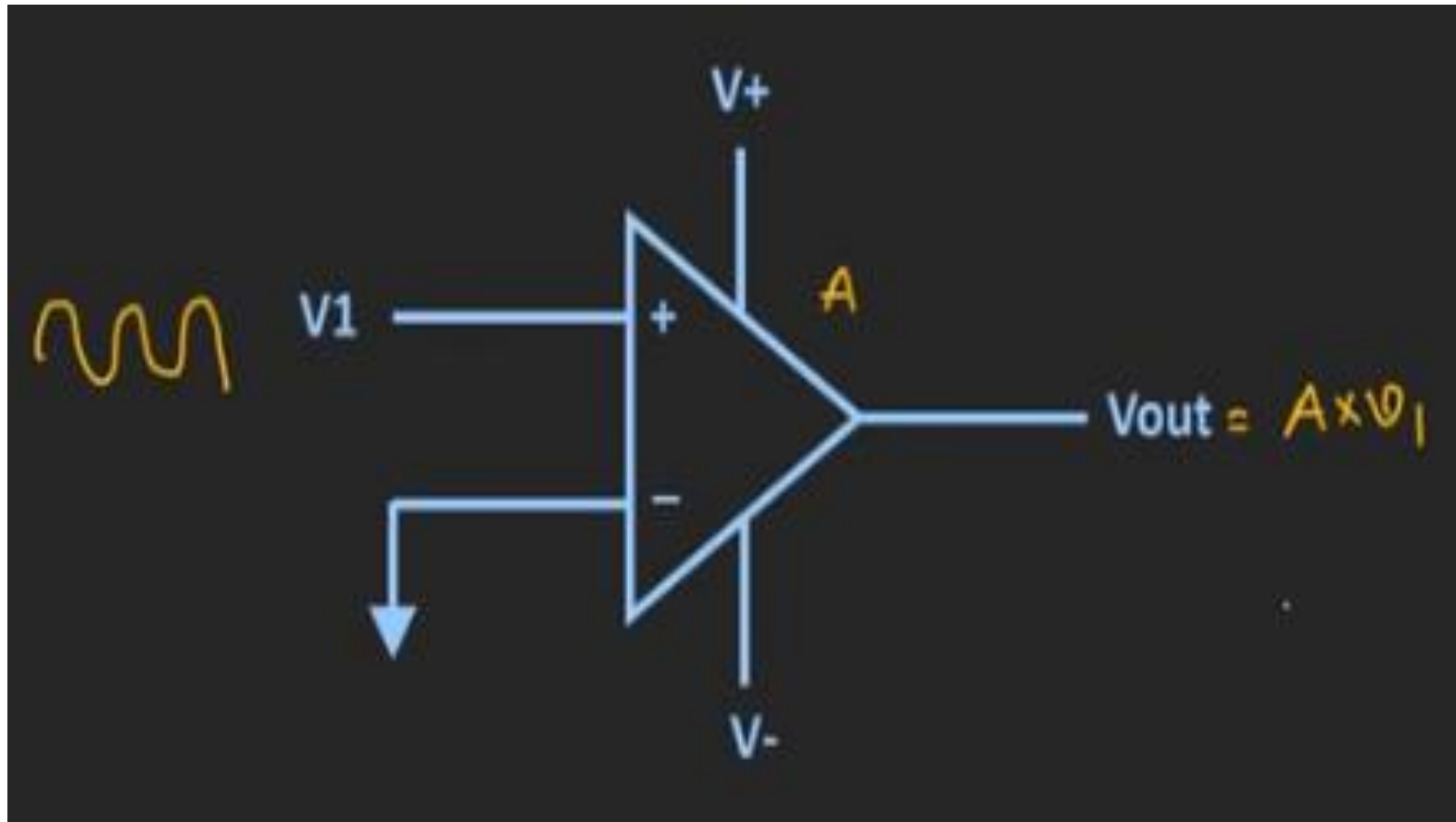

# Inverting Op-AMP

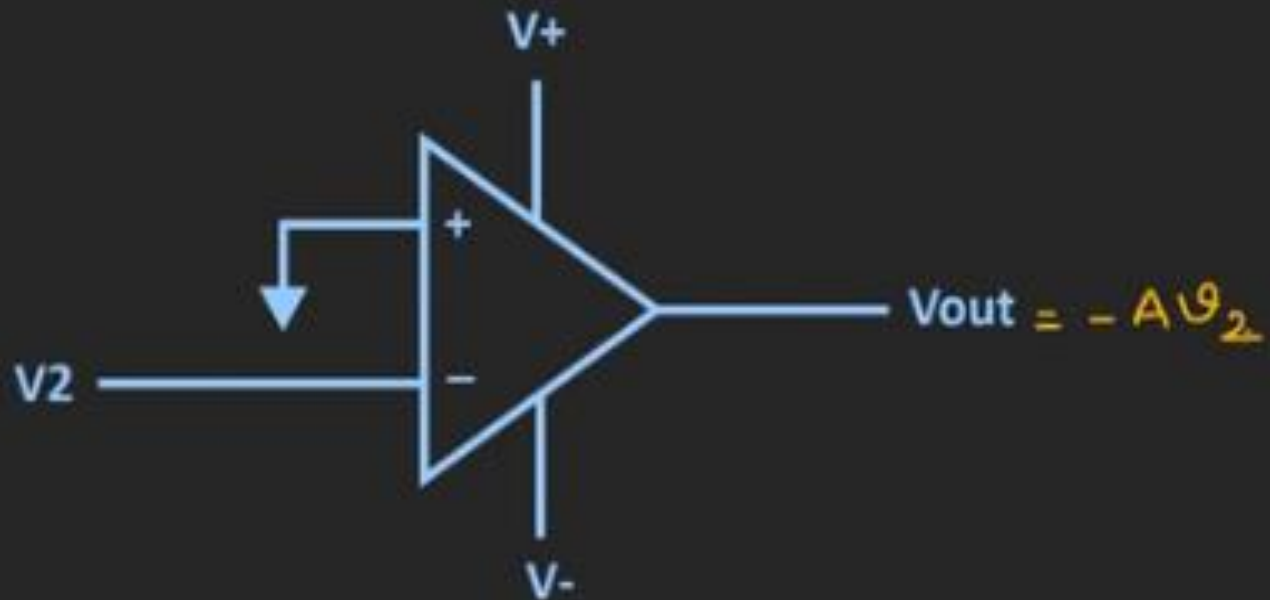


# Differential Op-AMP

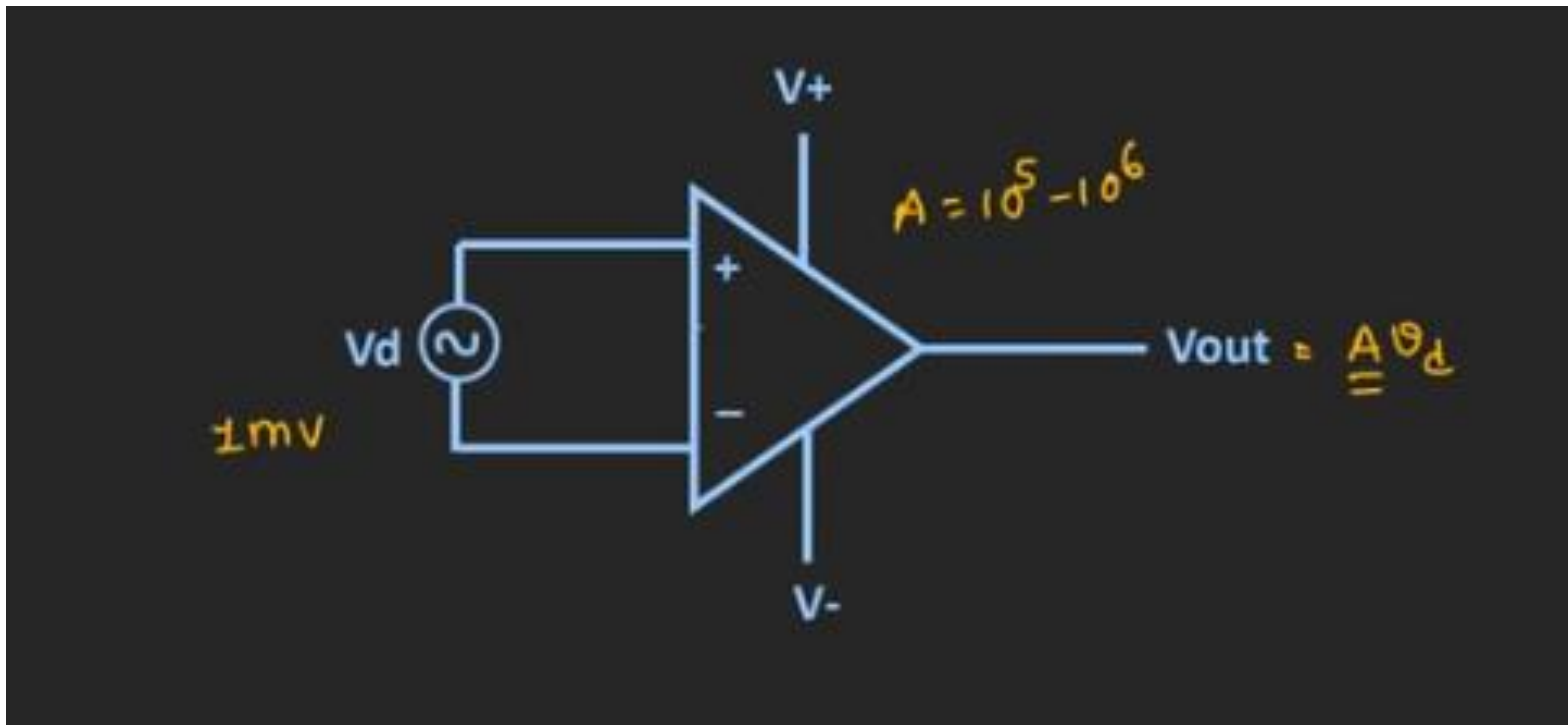

# Inverting/Noninverting Op-Amps


## Inverting Amplifier

$$V_o = -\frac{R_f}{R_1} V_1$$

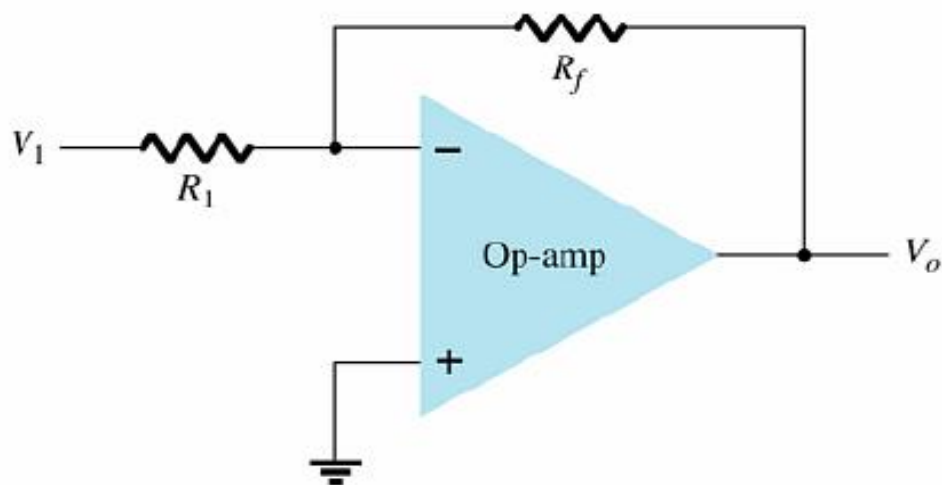

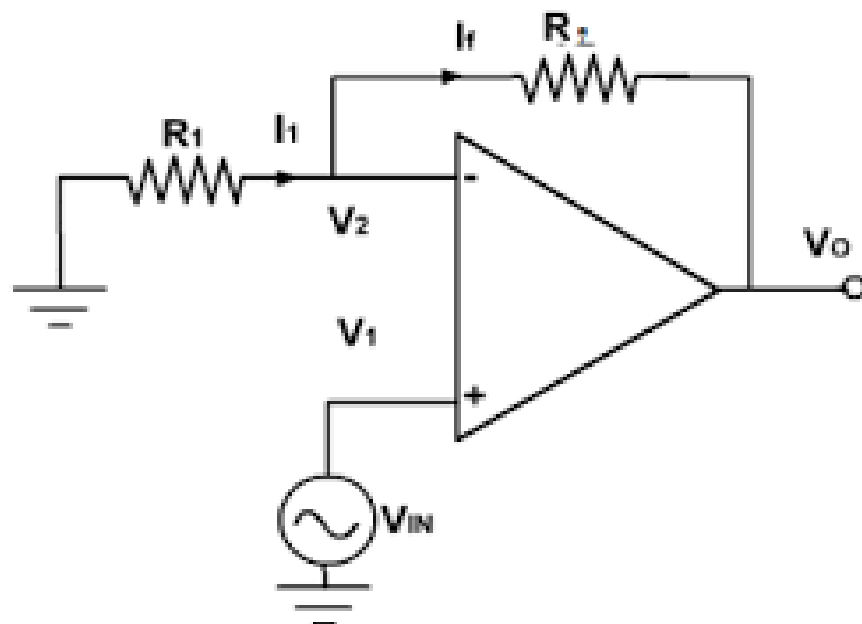
## Noninverting Amplifier


$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_1$$


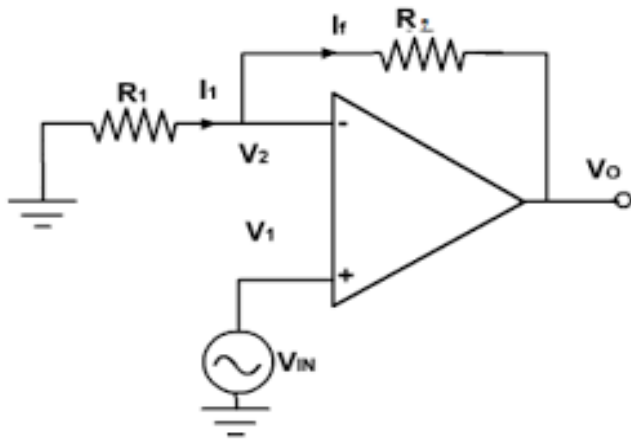
# Voltage Follower or Unity Gain Amplifier



$$A = 1 + \frac{R_f}{R_1}$$

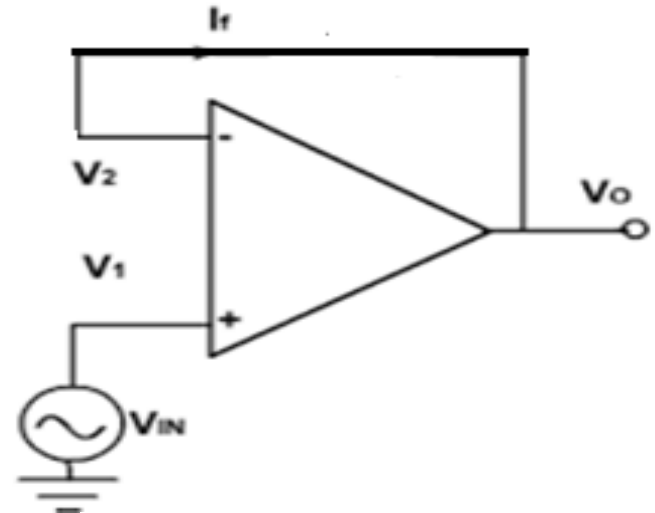


$$A = 1 + \frac{0}{\infty}$$

$$V_o = V_{in}$$




# Summing Amplifier

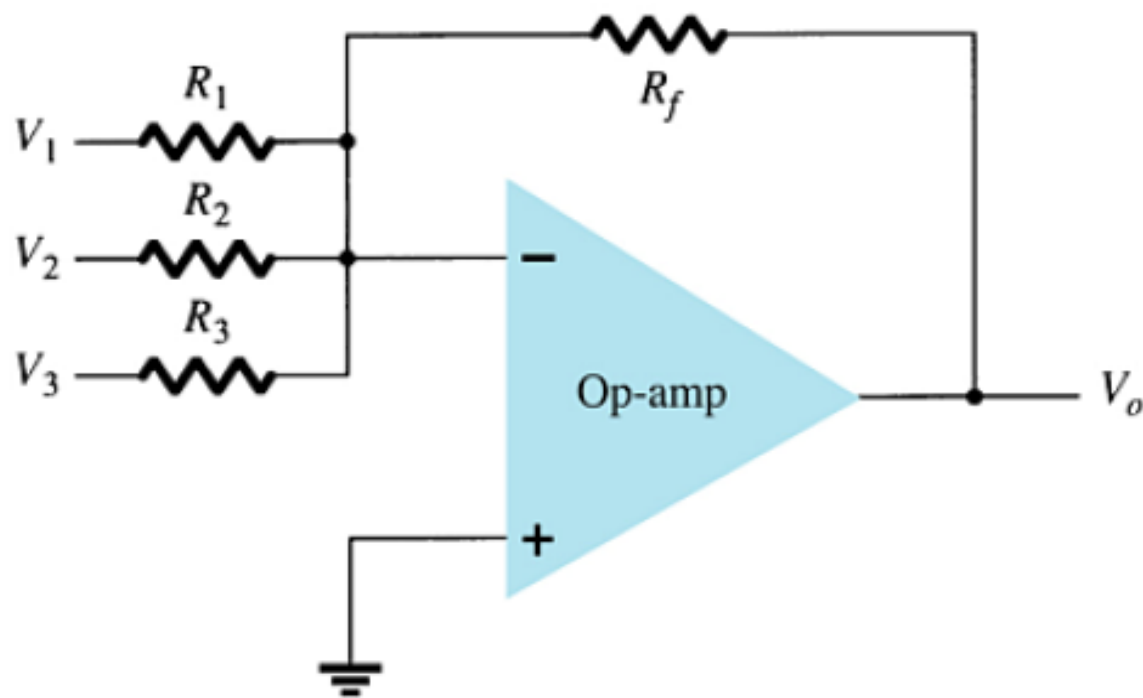

$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$

# Difference Amplifier or Subtractor

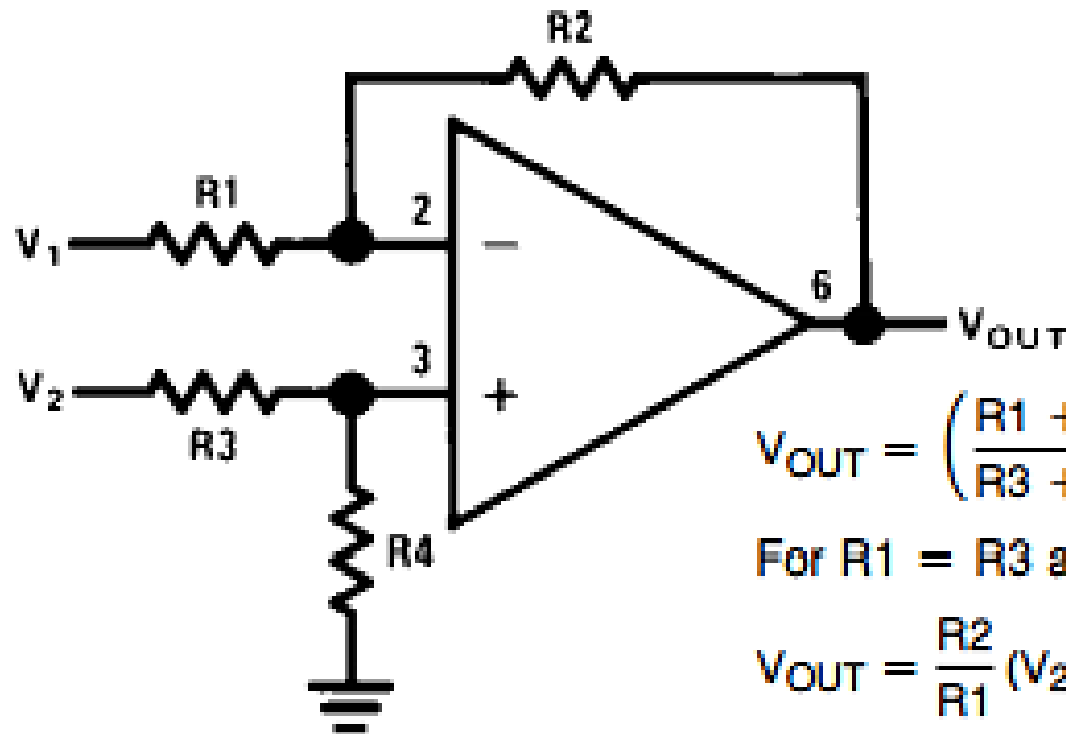


$$V_{OUT} = \left( \frac{R1 + R2}{R3 + R4} \right) \frac{R4}{R1} V_2 - \frac{R2}{R1} V_1$$

For  $R1 = R3$  and  $R2 = R4$

$$V_{OUT} = \frac{R2}{R1} (V_2 - V_1)$$
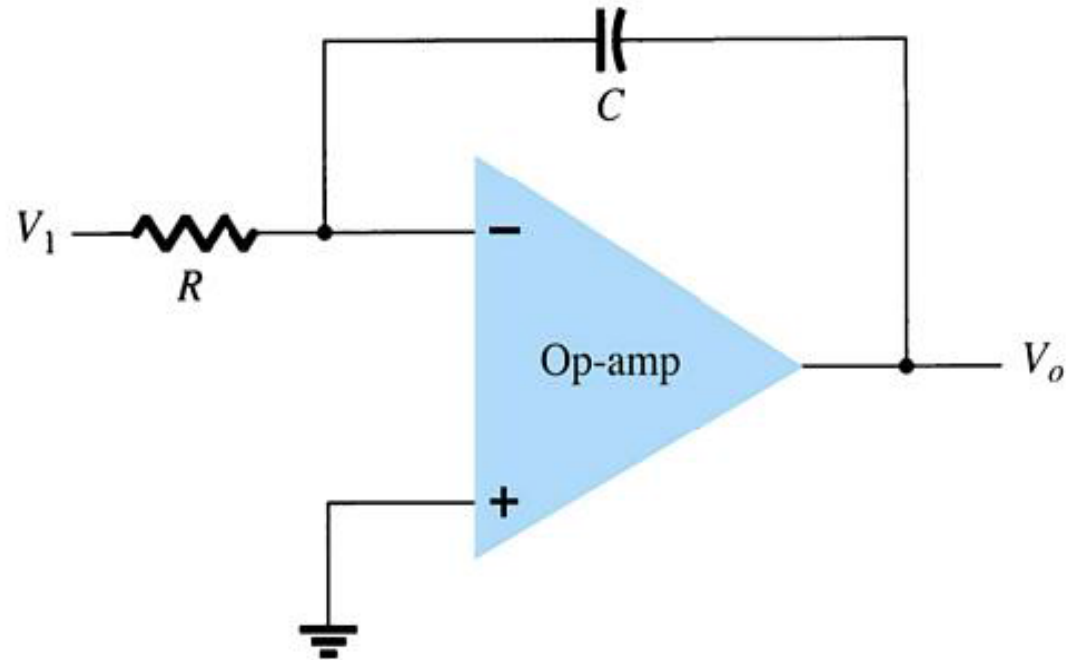
# Integrator


- The output is the integral of the input.
- This circuit is useful in low-pass filter circuits.



$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$
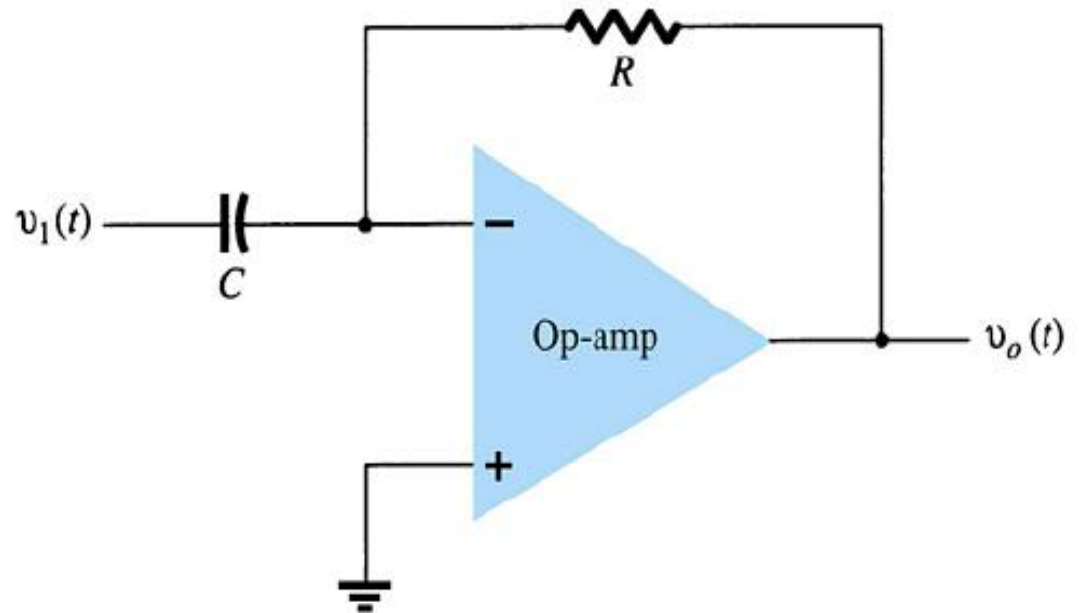
# Differentiator


- The differentiator takes the derivative of the input.
- This circuit is useful in high-pass filter circuits.




$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

# Tutorial Sheet

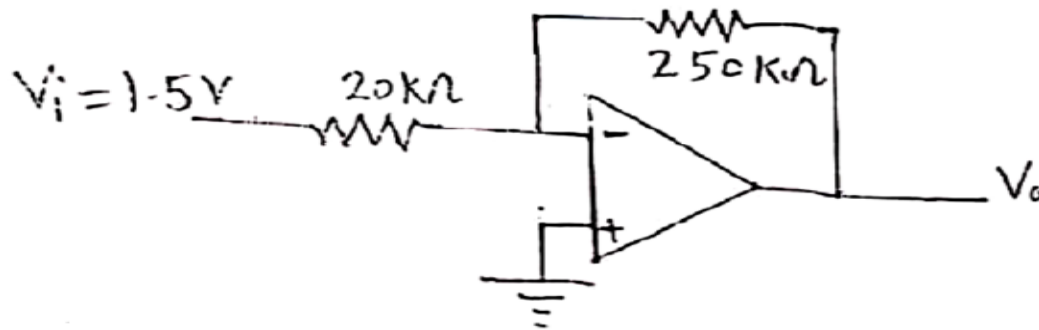
**Q1. Calculate the output voltage of the following op-amp circuit.**



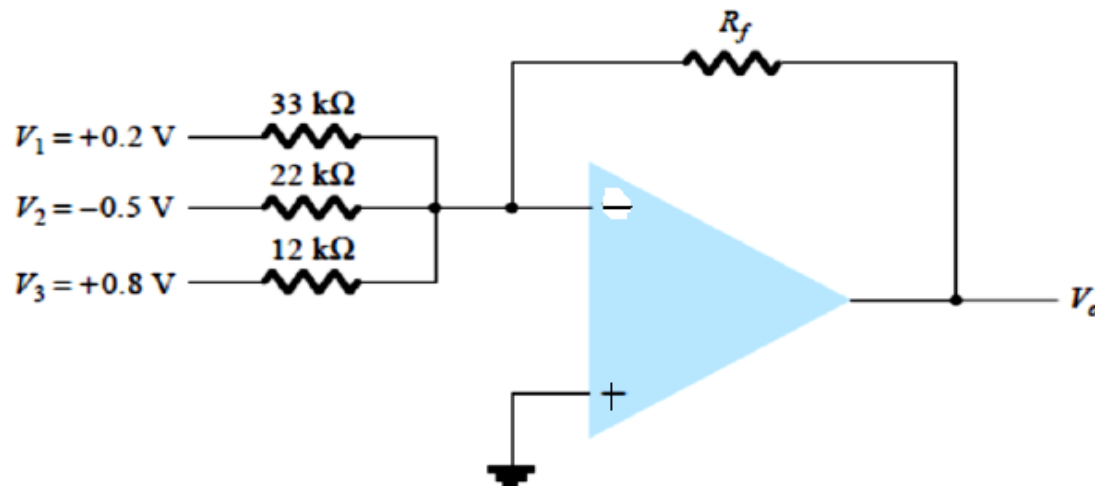
**Q2 Calculate the output voltage of summing amplifier for a)  $R_f = 330\text{ K}$ , b)  $R_f = 68\text{ K}$ .**



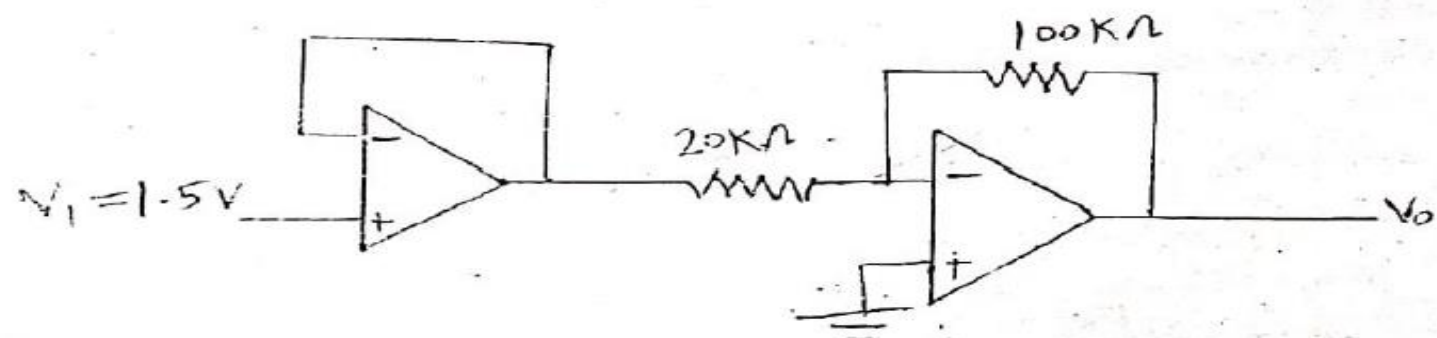Q3. Calculate the output voltage of the following op-amp circuit.




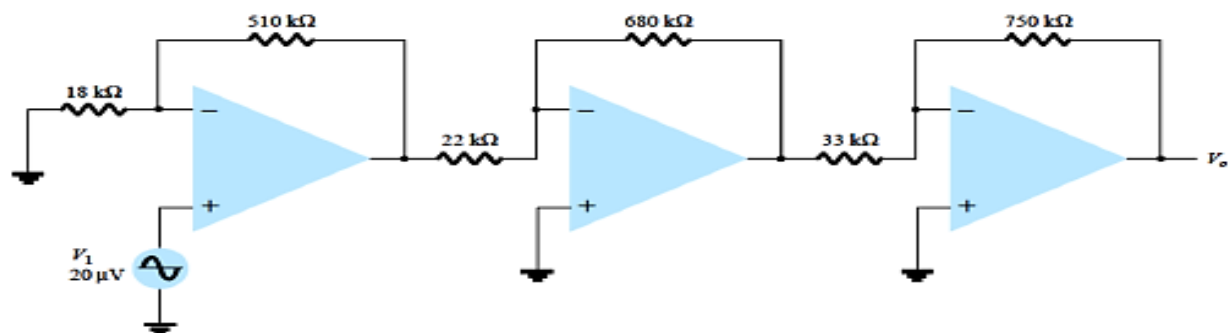Q4. Calculate the output voltage  $V_0$  of the following op-amp circuit.




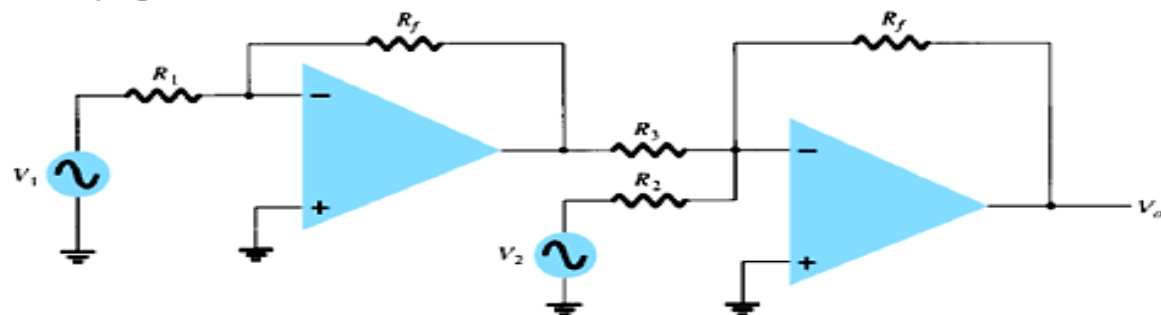Q5. Calculate the  $V_0$  and gain of each amplifier for the following op-amp circuit.

$R_f = 1\text{ M}\Omega$ ,  $R_1 = 100\text{ k}\Omega$ ,  $R_2 = 50\text{ k}\Omega$ , and  $R_3 = 500\text{ k}\Omega$ .  
 $V_1 = 4\text{ mV}$ ,  $V_2 = -2\text{ mV}$




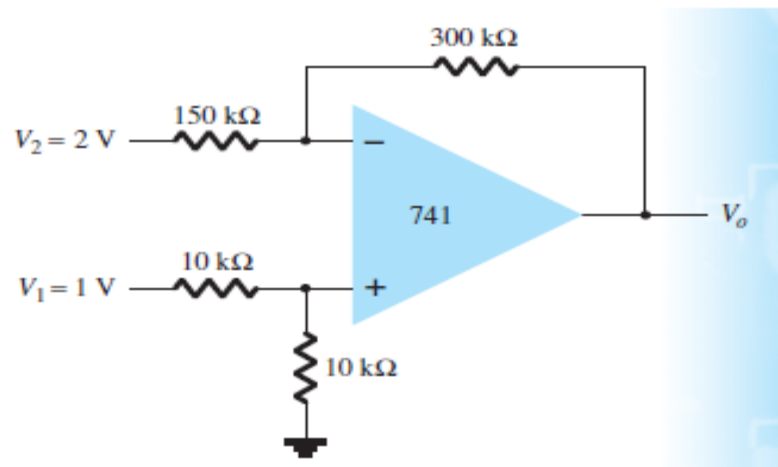**Q6. Calculate the output voltage of the following op-amp circuit.**



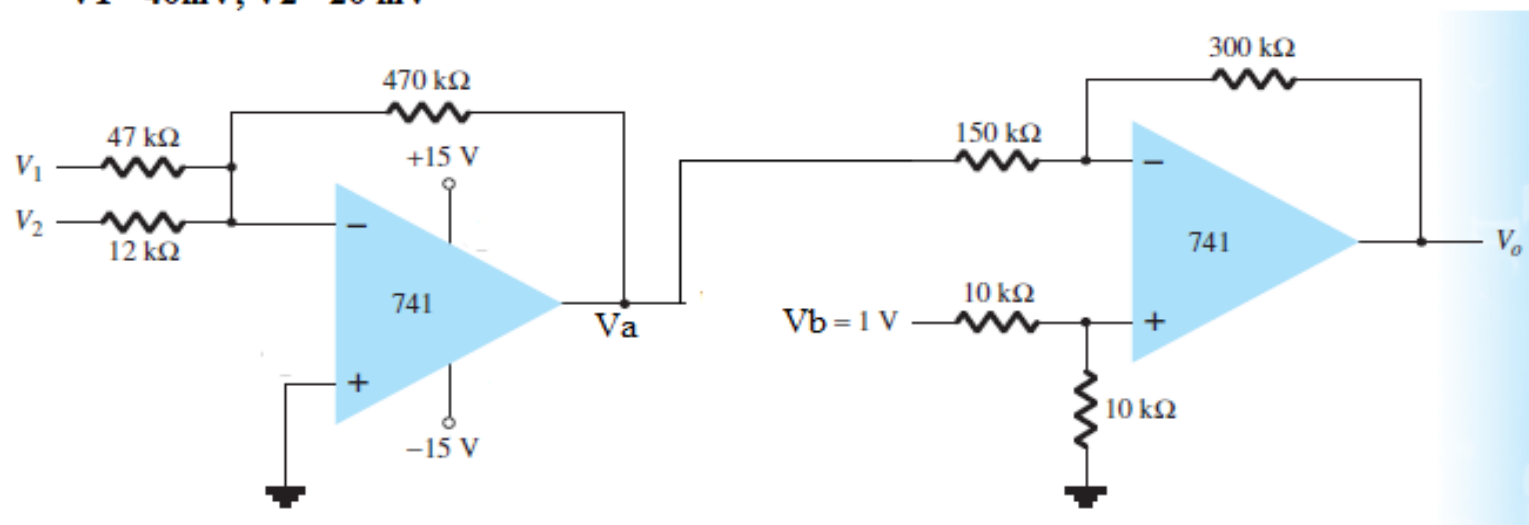**Q7. Calculate the output voltage of the following op-amp circuit.**

$V_1 = 40\text{ mV}$ ,  $V_2 = 20\text{ mV}$



# OP-AMP Characteristics

- **Open loop voltage gain**-It is the differential gain of an OP-AMP in the open loop mode of operation.
- **Input resistance**-It is defined as the equivalent resistance which can be measured at either at inverting or non-inverting terminal with the other terminal connected to ground.
- **Output resistance**-It is the resistance measured by looking into the output terminal of OP-AMP, with the input source short circuited.



- **Bandwidth**-It is the range over which all signal frequencies are amplified almost equally.
- **Common mode rejection ratio**-It is defined as the ratio of differential gain to common mode gain.
- **Slew rate**-It is defined as the maximum rate of change of output voltage per unit time.
- **Power supply rejection ratio**-It is the change in an OP-AMPs input offset voltage caused by variation in the supply voltage.