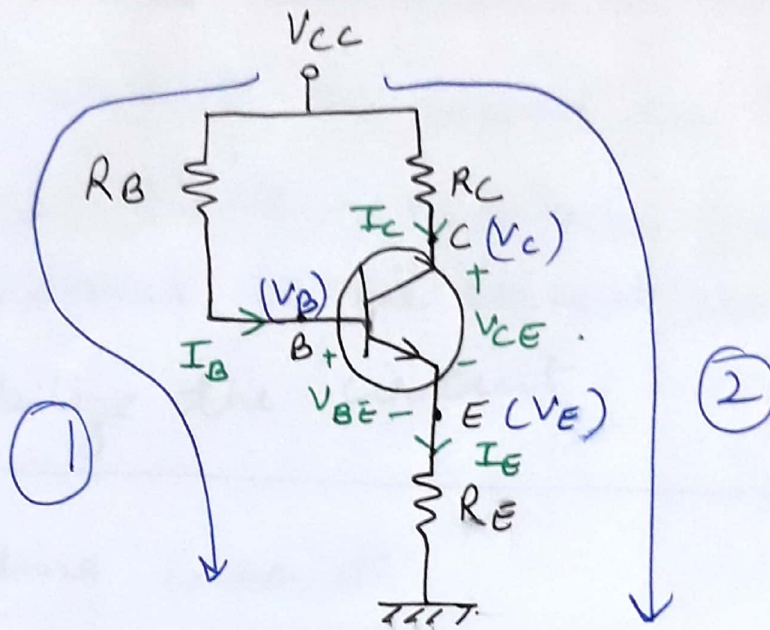


Emitter Bias (Self Bias)



* A resistance R_E has been added from emitter to the ground terminal in the fixed bias circuit. The remaining ckt is same as the fixed bias circuit.

* The Emitter resistance improves the bias stability as follows:-

→ If I_C increases $\Rightarrow I_E$ also increases

→ If I_E increases \Rightarrow Voltage $V_E = I_E R_E$ also increases.

\Rightarrow If V_E increases \Rightarrow Voltage $V_{BE} = V_{BE} + V_E$ increases as V_{BE} is fixed.

\Rightarrow if V_{BE} increases $\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B}$ decreases.

\Rightarrow if I_B decreases $\Rightarrow I_C = \beta I_B$ also decreases.

Thus, we can say that the increase in I_C will be compensated by the decrease in the value of I_B caused due to voltage (V_E) .

Hence, Emitter resistance provides negative feedback to the circuit and hence stabilize the circuit.

Finding Q-points

Applying KVL in loop ①

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

put $I_E = (\beta + 1) I_B$ ($\because I_E = I_B + I_C$
 $= I_B + \beta I_B$
 $= (\beta + 1) I_B$)

$$\Rightarrow V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$\Rightarrow \boxed{I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}} \quad \text{--- ①}$$

find
and $\boxed{\begin{aligned} I_C &= \beta I_B \\ I_E &= (\beta + 1) I_B \end{aligned}} \quad \text{--- ②}$

Applying KVL in loop ②.

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0.$$

$$\Rightarrow \boxed{V_{CE} = V_{CC} - I_C R_C - I_E R_E} \quad (3)$$

or $\because I_C \approx I_E$

$$\Rightarrow \boxed{V_{CE} \approx V_{CC} - I_C (R_C + R_E)} \quad (4)$$

Stability factor (S).

$$\boxed{S = \frac{1 + \beta}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}}$$

To find $\frac{dI_B}{dI_C}$ for Emitter bias

we have,

$$V_{CC} - I_B R_B - V_{BE} - (I_B + I_C) R_E = 0$$

Differentiate the eq. w.r.t I_C .

$$\Rightarrow 0 - \frac{dI_B}{dI_C} R_B - 0 - \left(\frac{dI_B}{dI_C} + 1 \right) R_E = 0.$$

or $\boxed{\frac{dI_B}{dI_C} = \frac{-R_E}{R_B + R_E}}$

$$\Rightarrow S = \frac{1 + \beta}{1 - \beta \left(\frac{-R_E}{R_B + R_E} \right)}$$

$$S \approx \frac{1 + \beta}{1 + \frac{\beta R_E}{R_B + R_E}}$$

if $R_B \ll R_E$

$$\Rightarrow R_B + R_E \approx R_E$$

$$\Rightarrow S \approx \frac{1 + \beta}{1 + \beta}$$

$$\text{or } \boxed{S \approx 1}$$

Hence the stability factor of Emitter Bias circuit is very low as compared to the fixed bias circuit $(1 + \beta)$. Hence Emitter bias circuit provides high stability to the Transistor.