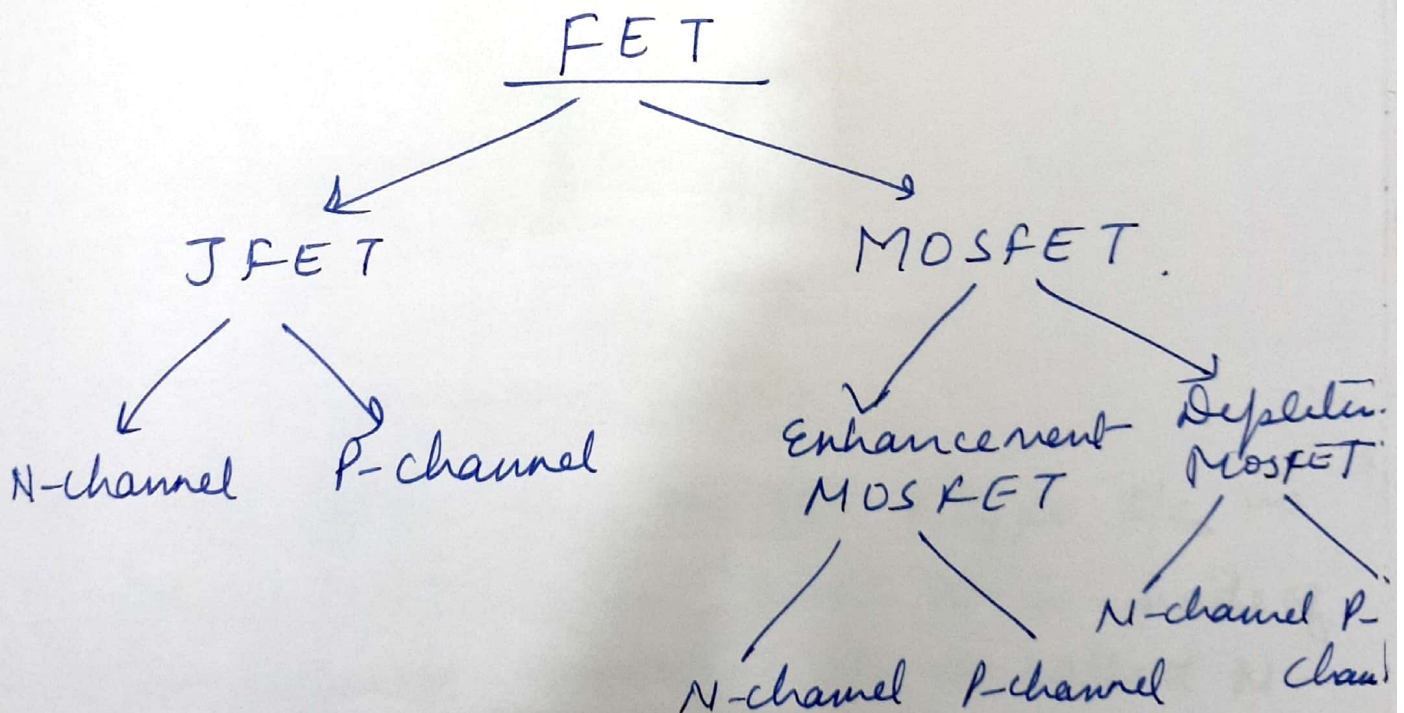


# Field Effect Transistor (FET)

Although BJT are used for amplification, it has some disadvantages like

- ① Very low Input Resistance
- ② Unstability ( $I_C = \beta I_B + (\beta + 1) I_{CO}$ )


Thus, we make a device which has high input resistance as well as in which the output current does not depend <sup>upon</sup> the leakage ~~current~~ current named as Field Effect Transistor (FET).


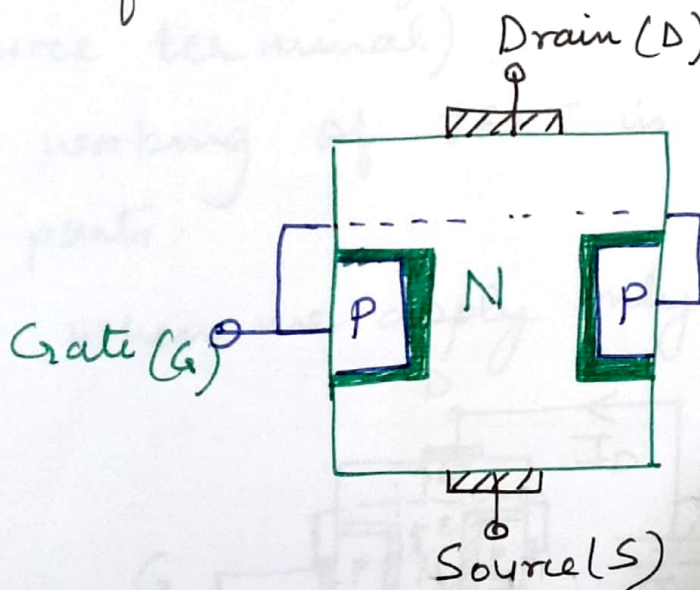
# N-Channel JFET (Junction Field Effect Transistor)

Construction :- For N-channel JFET,



we have an N-type s/c bar and made two metallic contacts with it named as drain (D) and ~~Gate (G)~~ Source (S). On the other side we dope two p-type s/c into the N-type which are connected together to form a terminal Gate (G).



- \* The path b/w the two P type s/c is called channel and since it is made of N-type s/c, therefore it is called N-channel JFET.
- \* There is a depletion layer b/w the P and N-type and hence no. current flows when there is no biasing.



## Symbol.

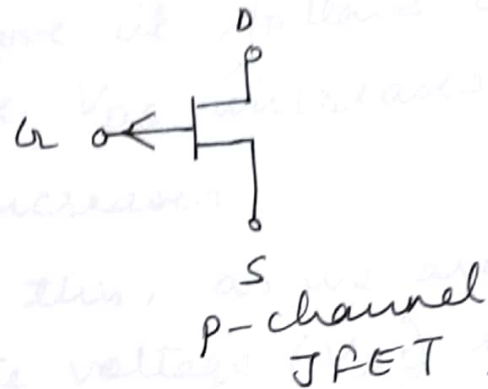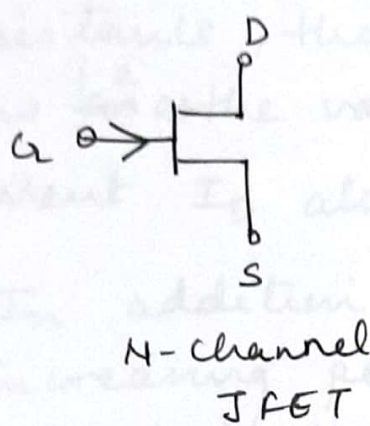


## Working.

We apply two voltage  $V_{GS}$  (voltage source between Gate and Source terminal) and  $V_{DS}$  (voltage source b/w Drain and Source terminal).

The working of JFET is divided into two parts.

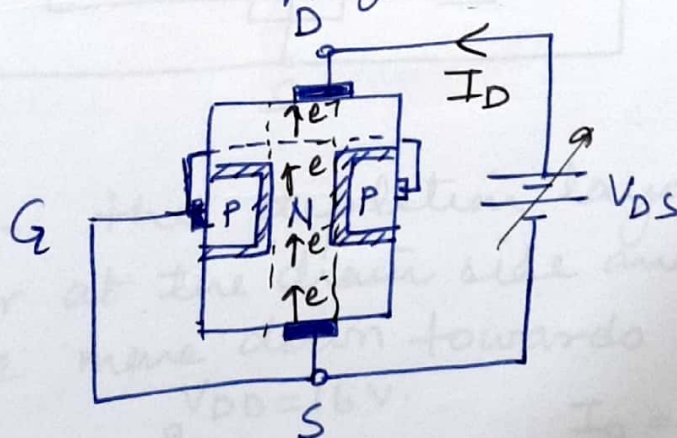1) when we apply only  $V_{DS}$  ( $V_{GS} = 0$ ).




(\* Note  $\rightarrow$  +ve terminal is Drain and -ve terminal is source for N-channel.)


\* The negative terminal of the drain source will emit the electrons which travel through the channel and reaches drain, hence we will say that a current  $I_D$  will flow through the channel from Drain to Source.

\* Since the n-type S/c acts as a resistance, therefore it follows Ohm's law <sup>i.e.</sup> as the voltage  $V_{DS}$  increases the current  $I_D$  also increases.

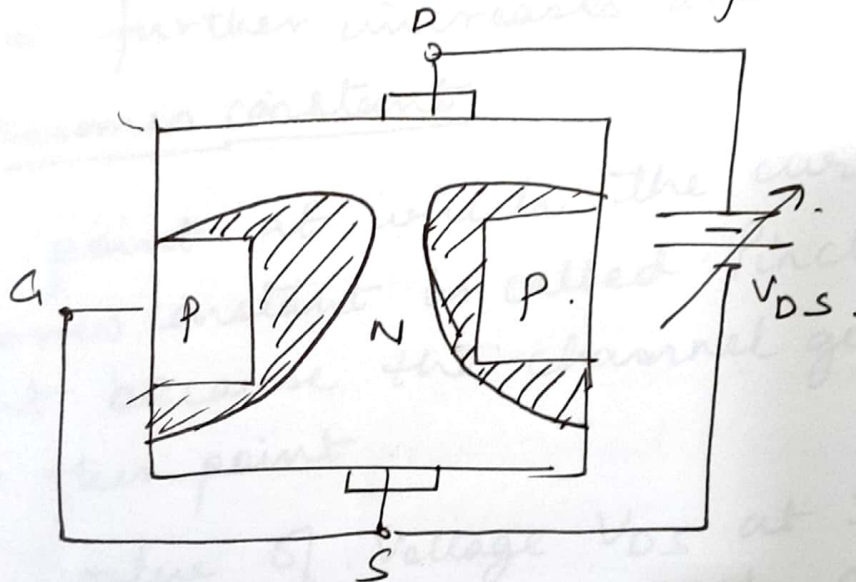\* In addition to this, as we are increasing positive voltage ( $V_{DS}$ ) in the N-type S/c bar, thus the P-N junction depletion layer at the junction of P-N type S/c also increases as it reverse bias the P-N junction.



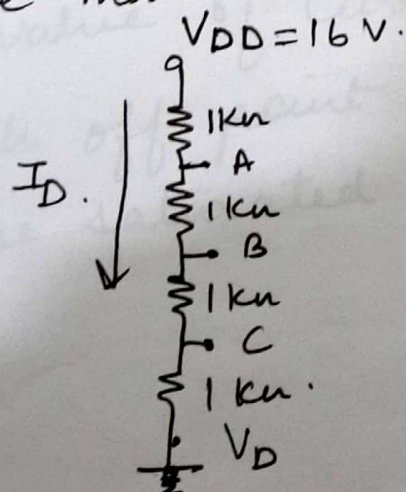Note: - the depletion layer width is higher at the drain side and gets narrower as we move down towards source.



$$I_D = \frac{16}{4} = 4 \text{ mA}$$

$$V_A = 16 - 4 \times 1 = 12$$

$$V_B = 16 - 4 \times 2 = 8$$

$$V_C = 16 - 4 \times 3 = 4$$

$$V_D = 16 - 4 \times 4 = 0$$



Thus it shows that as we move down the positive voltage decreases, hence the depletion layer width is higher at drain side and lower at the source side.

- \* In this manner, as we keep on increasing  $V_{DS}$ ,  $I_D$  will increase and also the depletion layer width is increasing and a point will come at which the depletion layer from both sides touch each other and the current will no further increases and hence it becomes constant.

The point at which the current becomes constant is called Pinch off point because the channel gets pinched at this point.

- \* The value of Voltage  $V_{DS}$  at the pinch off point is called pinch off Voltage ( $V_P$ ).

- \* The value of Current  $I_D$  at the pinch off point is called Drain to source saturated current ( $I_{DSS}$ ).



2) when  $V_{GS} \neq 0V$ .


\* Here,  $V_{GS}$  is always (-ve) voltage; ~~so that~~  
(Since Gate is made up of p-type S/C).  
Thus, P-N junction will always be reverse  
bias and hence, the input resistance will  
be very large.

When, we apply negative voltage to the  
Gate, it will promote the formation of  
depletion layer at the P-N junction along  
with  $V_{DS}$  and due to this the pinch-off  
condition becomes at the less voltage of  
 $V_{DS}$  than the earlier (when  $V_{GS} = 0V$ ) or  
we can say that the value of  $I_{DSS}$  decreases.


As we keep on increasing -ve voltage  
on the Gate, a point will come at which  
 $I_D$  becomes zero. This is known as cut-off  
point and the value of  $V_{GS}$  is denoted  
as  $(V_{GS\ off})$ .

Note that.

$$V_{GS\ off} = -V_p$$

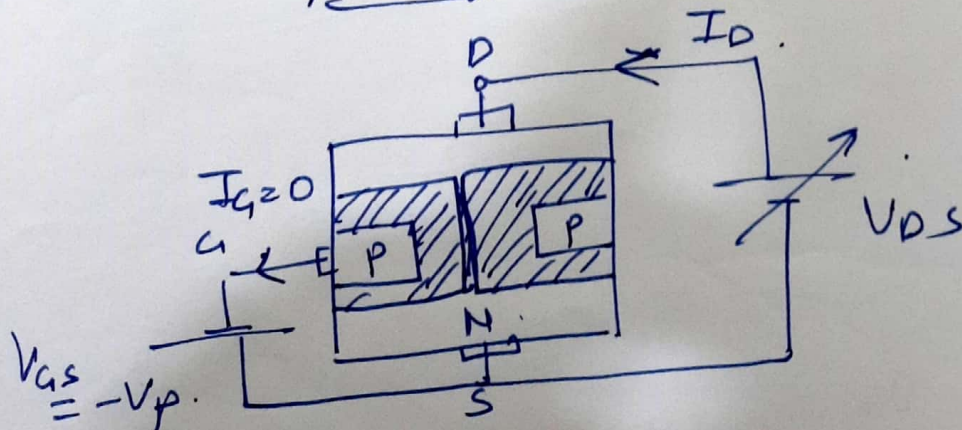

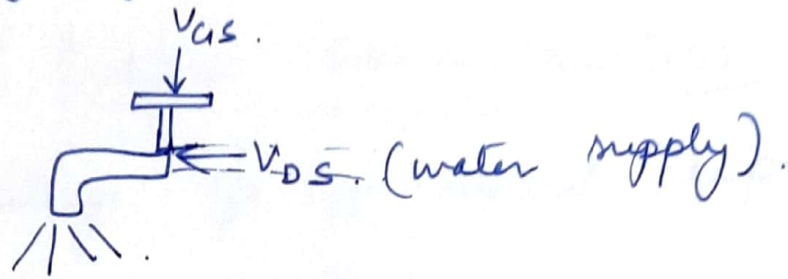\* The Working of JFET is similar to a Tap.



As the tap control the intensity of water coming out. Similarly  $V_{GS}$  control the amount of  $I_D$  (drain current) and hence JFET is known as Voltage Control device.

Relation b/w current and Voltage

The relation is given by Shockley equation

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

where  $I_D \rightarrow$  drain current

$I_{DSS} \rightarrow$  Maximum drain current

$V_{GS} \rightarrow$  Applied gate to source voltage


$V_P \rightarrow$  pinch off voltage



# Characteristics of JFET (n-channel)
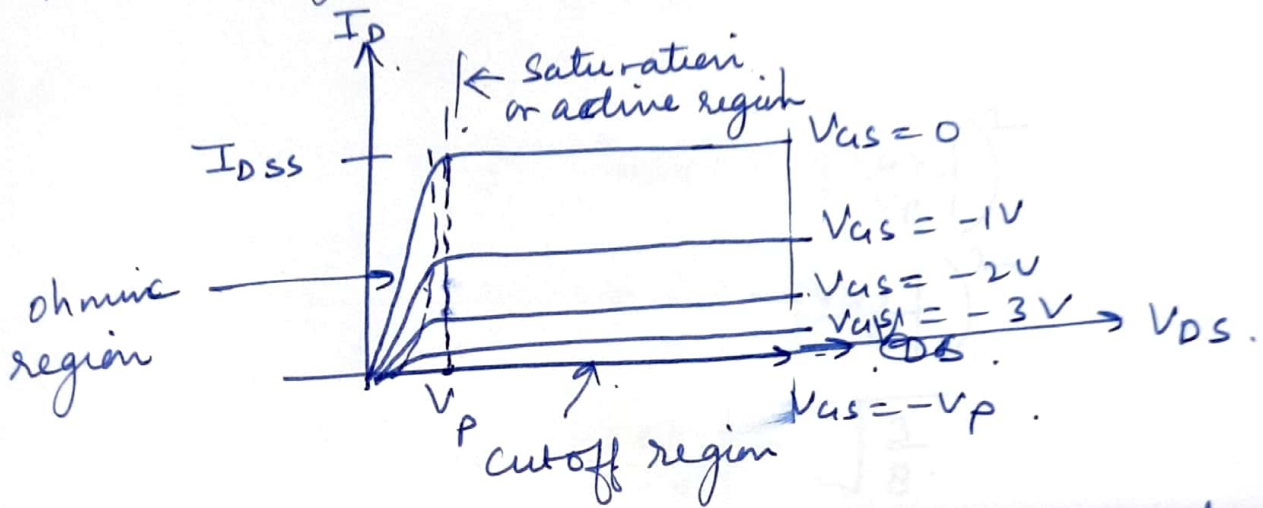
## 1) Transfer Output characteristics


o/p voltage  $V_D$  vs o/p current keeping input voltage as constant


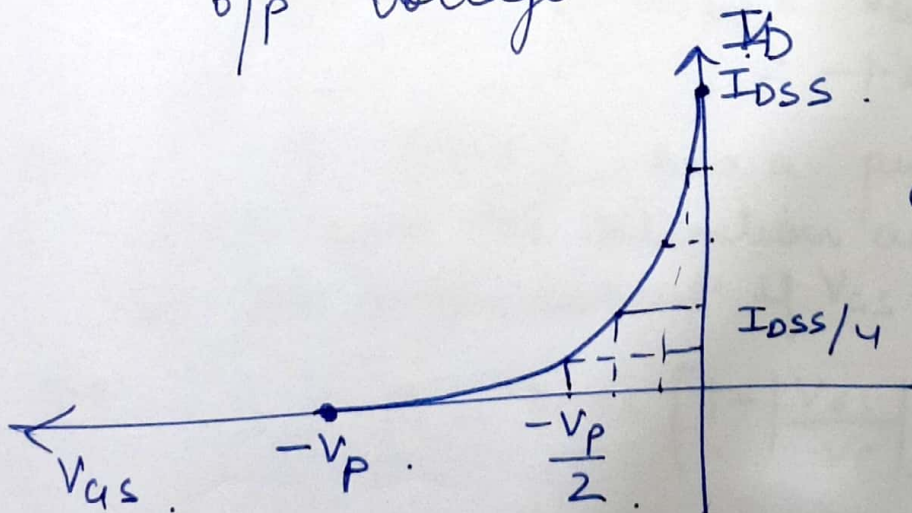
## 2) Transfer characteristics (Transconductance)

o/p voltage  $V_D$  vs o/p current keeping o/p voltage constant

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$





## Numericals

Q1. An n-channel JFET has  $I_{DSS} = 8 \text{ mA}$  and  $V_p = -4 \text{ V}$ .

- (a) if  $I_D = 3 \text{ mA}$  Calculate the value of  $V_{GS}$   
(b) Calculate  $V_{DS(sat)}$  for  $I_D = 3 \text{ mA}$ .

Sol<sup>n</sup>. we have

$$(a) \quad I_D = I_{DSS} \left( 1 - \left| \frac{V_{GS}}{V_p} \right| \right)^2$$

$$(2) \quad 3 = 8 \left( 1 - \left| \frac{V_{GS}}{-4} \right| \right)^2$$

$$\Rightarrow \quad 1 - \left| \frac{V_{GS}}{-4} \right| = \sqrt{\frac{3}{8}}$$

$$V_{GS} = -4 \left( 1 - \sqrt{\frac{3}{8}} \right) \\ = -1.55 \text{ V.}$$

(b) To Calculate  $(V_{DS})_{sat}$

$$(V_{DS})_{sat} = V_{GS} - V_p \\ = -1.55 + 4 = 2.45 \text{ V.}$$

Q2 :- A JFET has a pinch-off voltage of  $-4 \text{ V}$ . and the saturation current of  $9 \text{ mA}$ . Calculate the drain current if  $V_{GS} = -2 \text{ V}$ .

Ans. 
$$I_D = I_{DSS} \left( 1 - \left| \frac{V_{GS}}{V_p} \right| \right)^2 = 9 \left[ 1 - \frac{2}{4} \right]^2 \\ = \frac{9}{4} = 2.25 \text{ mA}$$

Q3. A certain JFET has  $I_{DSS} = 12 \text{ mA}$  and  $V_p = -6 \text{ V}$ . Calculate  $g_m$  (transconductance) for  $V_{GS} = -1 \text{ V}$ .

Sol. we have  $g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_p} \right)$

where  $g_{m0} = \frac{-2 I_{DSS}}{V_p}$

$$= \frac{-2 \times 12}{-6} = 4 \text{ mA/V}$$

$$g_m = 4 \left[ 1 - \frac{(-1)}{(-6)} \right] = \frac{4 \times 5}{6}$$

$$= 3.33 \text{ mS}$$



## Parameters of JFET

1. Dynamic drain resistance ( $r_d$ )  $\rightarrow$  It is the AC resistance of a JFET. It is defined as ratio of change in output voltage (drain voltage) to change in output current (drain current)  $I_D$  at a constant value of gate to source voltage ( $V_{GS}$ ).

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{\text{const. } V_{GS}}$$

2. Transconductance ( $g_m$ )

It is ratio of change in ~~s/p voltage~~ o/p current ( $I_D$ ) to change in s/p voltage ( $V_{GS}$ ).

$$g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{\text{const. } V_{DS}}$$

Derivation for  $g_m$ .

we have  $I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$

differentiate w.r.t  $V_{GS}$ .

$$\frac{dI_D}{dV_{GS}} = \frac{-2I_{DSS}}{V_P} \left( 1 - \frac{V_{GS}}{V_P} \right)$$

$$\text{or } g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_P} \right)$$

where  $g_{m0} = \left| \frac{2I_{DSS}}{V_P} \right|$

### 3. Amplification factor ( $\mu$ ).

Ratio of change in o/p voltage to change in i/p voltage.

$$\boxed{\mu = \frac{\Delta V_{DS}}{\Delta V_{GS}}}_{I_D = \text{const.}}$$


Relation b/w.  $\mu$ ,  $g_m$  and  $r_d$ .

we have

$$\mu = \frac{\Delta V_{DS}}{\Delta V_{GS}} \cdot \frac{\Delta I_D}{\Delta I_D}$$
$$= \left( \frac{\Delta V_{DS}}{\Delta I_D} \right) \cdot \left( \frac{\Delta I_D}{\Delta V_{GS}} \right)$$

$$\boxed{\mu = r_d \times g_m}$$

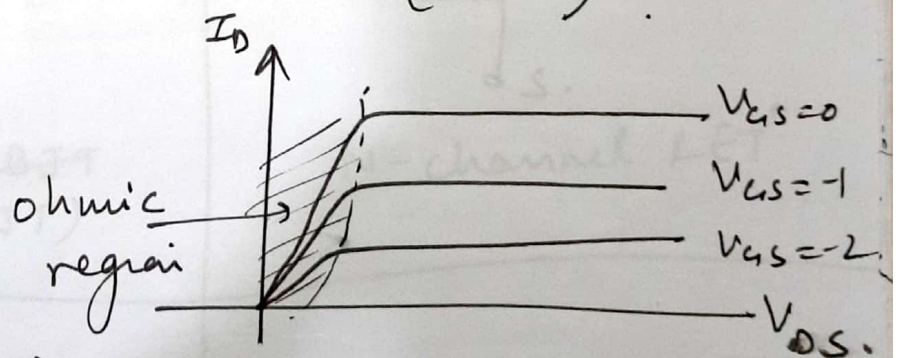\* Note FET is ~~also~~ also known as voltage variable resistor (VVR).



In ohmic region, the JFET acts as resistance. and its value changes as we change the value of  $V_{GS}$ .

$$\boxed{r_d = \frac{r_{d0}}{\left(1 - \frac{V_{GS}}{V_P}\right)^2}}$$