
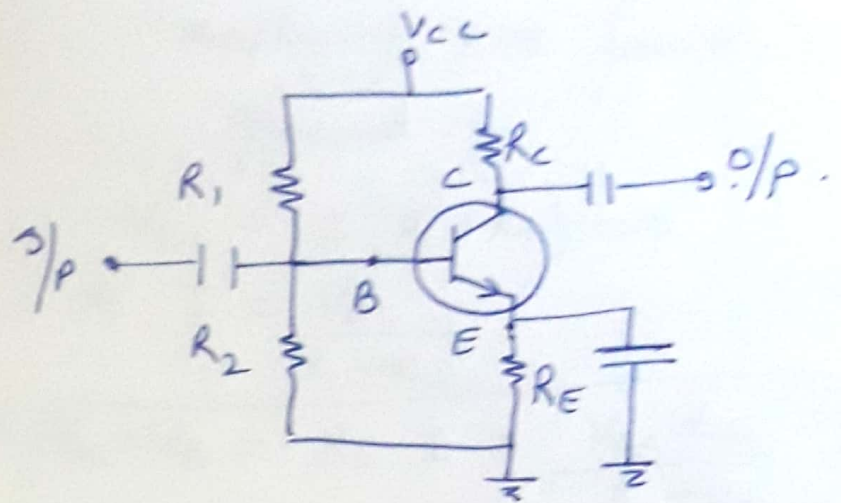



Voltage Divider Bias

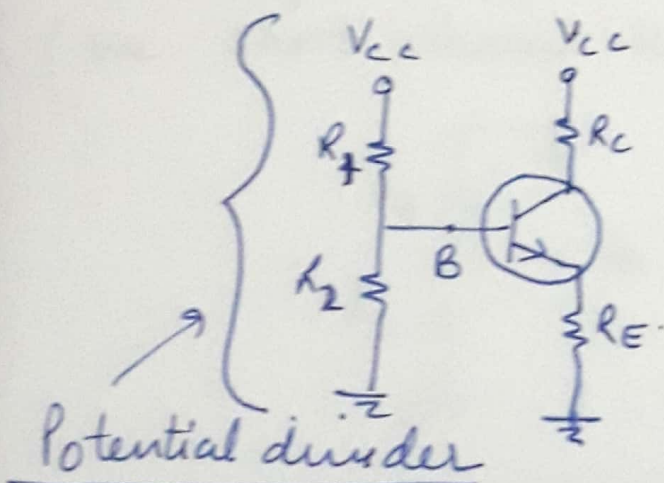


It can be simplified as: -



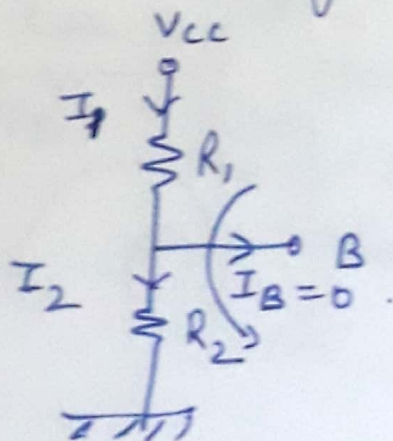We make equivalent circuit of the potential divider by using Thevenin's theorem.



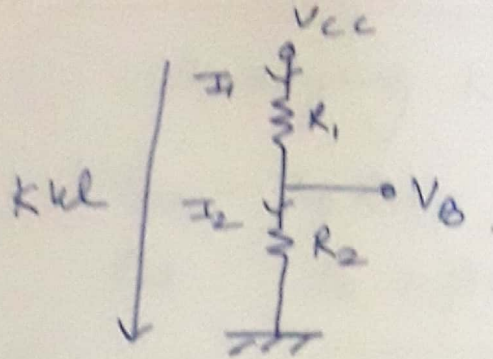To find Equivalent Voltage (Thevenin Voltage) at Base. (V_{th})
(we open circuit the o/p)



$$\therefore I_B = 0$$

$$\Rightarrow I_1 = I_2 = I$$


Applying KVL from V_{CC} to ground.

$$V_{CC} - I(R_1 + R_2) = 0$$

$$\Rightarrow I = \frac{V_{CC}}{R_1 + R_2}$$

$$\text{and } V_{th} = V_B = R_2 \cdot I = \frac{V_{CC} R_2}{R_1 + R_2}$$

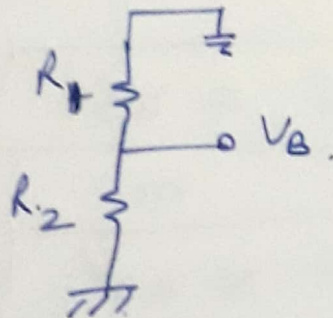
To find Equivalent resistance (R_{th}).
(we short circuit the Voltage source.)



R_1 and R_2 becomes in parallel.

$$\Rightarrow R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

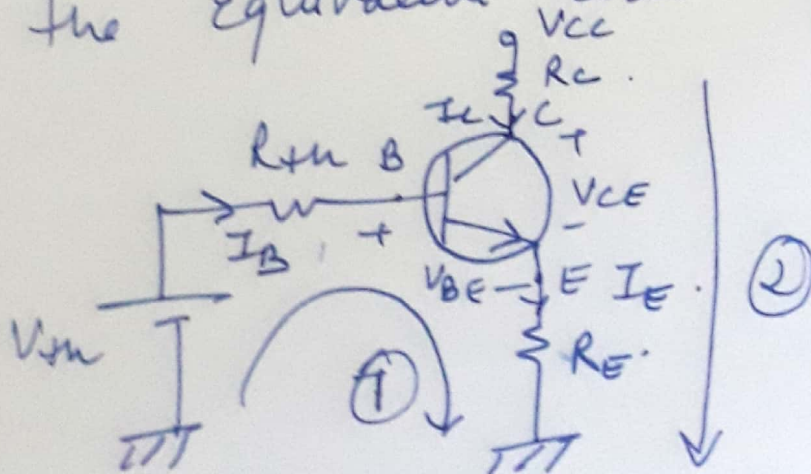Now the Equivalent circuit of the V_{DB} will be.



Applying KVL in loop ①

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0.$$

Put $I_E = (\beta + 1) I_B$.

$$\textcircled{1} \Rightarrow \boxed{I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}}$$

~~1~~ ②

$$\boxed{\begin{aligned} I_C &= \beta I_B \\ I_E &= (\beta + 1) I_B \end{aligned}}$$

③ Applying KVL in loop ②

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\Rightarrow \boxed{V_{CE} = V_{CC} - I_C R_C - I_E R_E}$$

or

$$\boxed{V_{CE} \approx V_{CC} - I_C (R_C + R_E)}$$